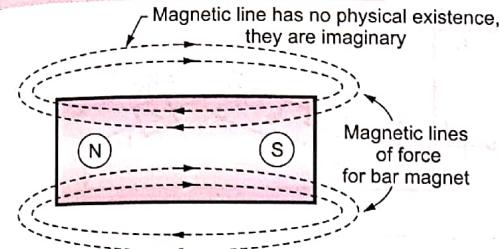


Exam Preparation Chart



Chapter 1 (Unit I)

Electromagnetism

Bar magnet - Magnetic lines of force




Right hand thumb rule

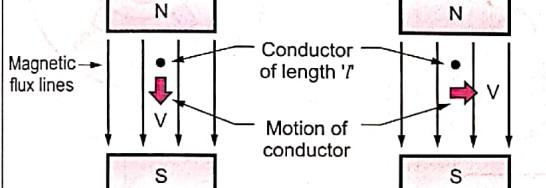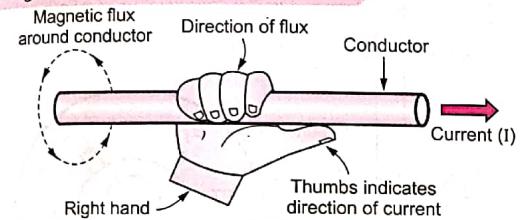


(a) Conductor moving in magnetic field

(b) Perpendicular motion of conductor

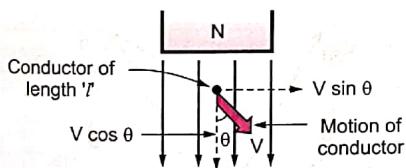


(c) Conductor making an angle


Dot and cross convention

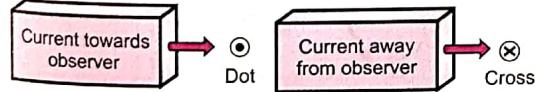

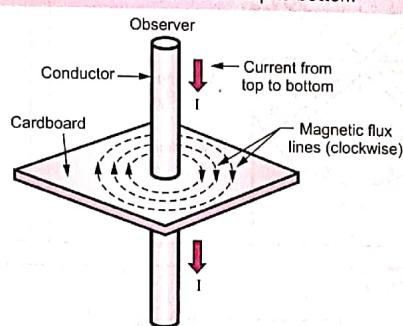
Conductor carries current from top to bottom



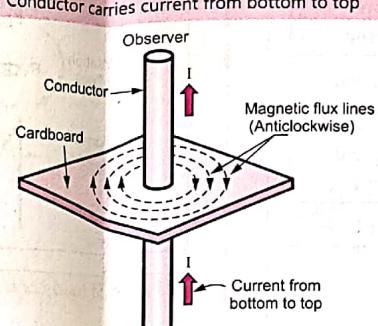Conductor carries current from bottom to top




Permanent magnet

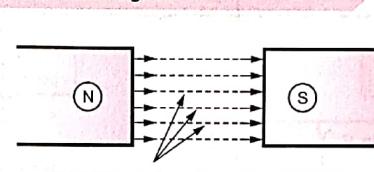


Magnetic flux lines in permanent magnet


Force on current carrying conductor

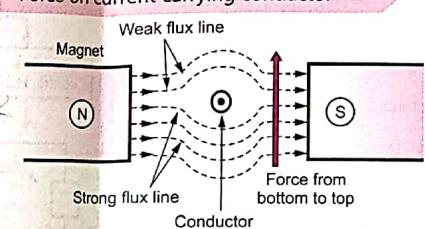


Fleming's left hand rule

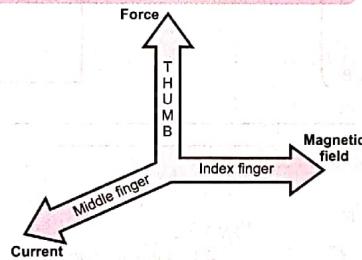


Fleming's left hand rule

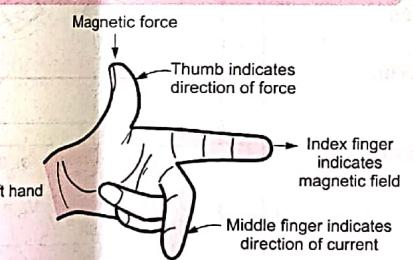

Series magnetic circuit

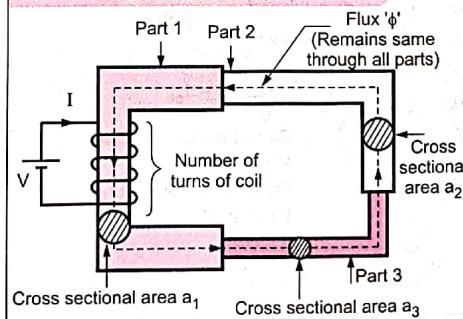

Energy stored in magnetic field

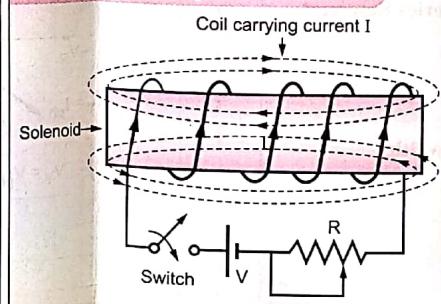

Important Formulae

$$1. \text{ Absolute Permeability } (\mu) \quad \mu = \frac{B}{H}$$

Where, B = magnetic flux density
 H = magnetic field strength

$$2. \text{ Permeability of Vacuum or Free Space } (\mu_0)$$

$$\mu_0 = \frac{B}{H} \text{ in vacuum or free space} = 4\pi \times 10^{-7} \text{ H/m}$$

Where, B = magnetic flux density,
 H = magnetic field strength

$$3. \text{ Magnetic Permeability}$$

$$\therefore \mu = \mu_0 \mu_r$$

Magnetic permeability Relative permeability
 Permeability of free space

$$4. \text{ Magnetomotive Force (MMF)}$$

$$\therefore \text{mmf} = N \times I$$

Number of turns Current through the coil

$$5. \text{ Reluctance } s = \frac{l}{\mu a}$$

Here, l = Length of magnetic circuit in meter
 a = Cross-sectional area in (meter)²

and, μ = Permeability $\therefore s = \frac{\text{mmf}}{\phi}$

The magneto motive force is given by, $\text{mmf} = NI$

Number of turns of coil Current through coil
 $\therefore s = \frac{NI}{\phi} \text{ AT / Wb}$
 Magnetic flux

$$6. \text{ Equation of reluctance}$$

$$s = \frac{l}{\mu a}$$

mean length
 Permeability Cross sectional area

$$7. \text{ Total reluctance of series magnetic circuit with air-gap. } s_T = \frac{l_i}{\mu_0 \mu_r a} + \frac{l_g}{\mu_0 a}$$

8. The magnitude of force exerted on current carrying conductor, placed in magnetic field, is given by

$$F = B I l$$

Mechanical force Active length of conductor
 Current through conductor Magnetic flux density

$$9. \text{ If a conductor is inclined and it makes an angle '}\theta\text{' with respect to axis of magnetic field then force is given by, } F = BI l \sin \theta$$

$$10. \text{ Faraday's Second Law}$$

$$\therefore e = N \frac{d\phi}{dt}$$

Number of turns of coil Rate of change of flux

$$11. \text{ Lenz's Law}$$

$$\therefore e = N \frac{d\phi}{dt}$$

Induced emf Number of turns of coil
 Change in flux

Negative sign indicates opposition to cause producing current

$$12. \text{ Mathematical Eqn. of Dynamically Induced emf}$$

$$\therefore e = B l V$$

Induced emf Velocity of conductor
 Length of conductor
 Flux density

$$13. \text{ Dynamically induced emf } e = Bl V \sin \theta$$

Perpendicular component of V

$$14. \text{ Equation of self inductance } e = -L \frac{dI}{dt} \text{ Volts}$$

$$15. \text{ Another Equation of Self Inductance } \therefore L = \frac{N^2 \mu_0 \mu_r a}{l} \text{ Henry}$$

$$16. \text{ Equation of mutually induced emf in terms of mutual inductance } e_2 = -M \frac{dI_1}{dt} \text{ Volts}$$

$$17. \text{ Coefficient of Coupling (k) } M = k \sqrt{L_1 L_2}$$


$$18. \text{ Energy Stored in Magnetic Field } \therefore E = \frac{LI^2}{2}$$

$$19. \text{ Equation of energy stored per unit volume } \therefore E = \frac{1}{2} \mu_0 \mu_r H^2 = \frac{1}{2} \mu H^2$$


Chapter 2 (Unit II)

Electrostatics

Flux lines from $+Q$ to $-Q$

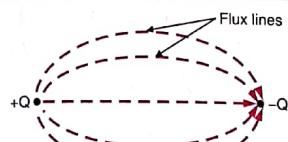

Construction of Capacitor

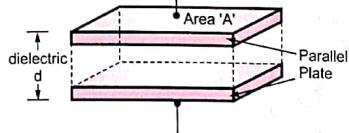

Important Formulae

$$\text{Electric flux density} = \frac{\text{Electric flux}}{\text{Surface area}}$$

Relationship between 'D' and 'E'

$$D = \epsilon E, \quad \text{But } \epsilon = \epsilon_0 \epsilon_r, \\ \therefore D = \epsilon_0 \epsilon_r E$$

Coulomb's Law

$$F = K \cdot \frac{Q_1 Q_2}{R^2}$$

Here, F = Force in Newton

Q_1 and Q_2 = Point charges in Coulomb's

K = Constant of proportionality

R = Distance between Q_1 and Q_2 in meters

Capacitance

$$\text{Capacitance} = C = \frac{\text{Charge}}{\text{Voltage}}$$

(coulombs)
(volts)

Capacitance of Parallel Plate Capacitor

$$C = \epsilon_r \epsilon_0 \frac{A}{d} \text{ Farad}$$

Capacitor in Series

The equivalent capacitance C_s of n capacitors connected in series is given as,

$$\frac{1}{C_s} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} + \dots + \frac{1}{C_n}$$

Capacitors in Parallel

The equivalent capacitance C_p of n capacitors connected in parallel is given as,

$$C_p = C_1 + C_2 + C_3 + \dots + C_n$$


Energy Stored by a Capacitor

$$E = \frac{1}{2} QV = \frac{1}{2} CV^2 \text{ (Joules)}$$


Chapter 3 (Unit II)

AC Fundamentals

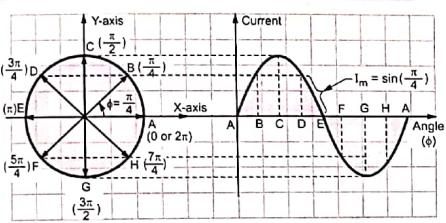
Phasor rotates in anticlockwise direction




Cycle

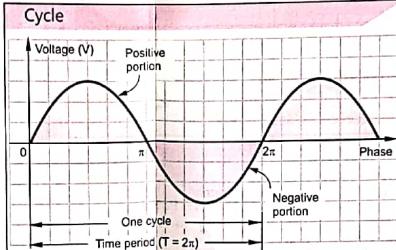


Average value

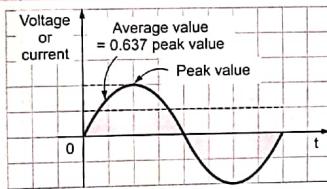


Phase difference

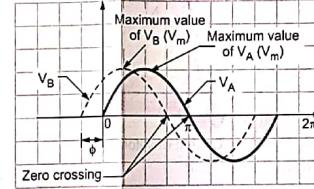


Generation of alternating voltage

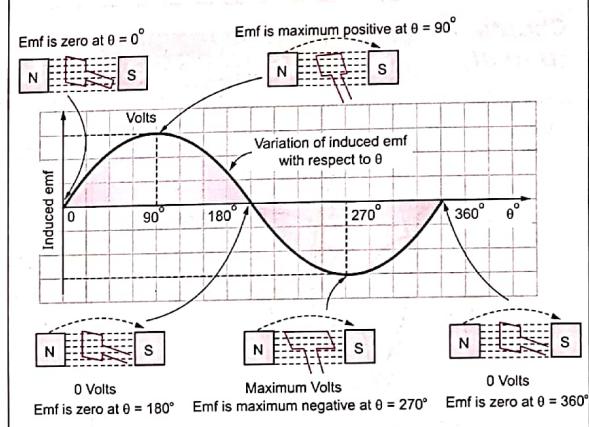

Voltage waveform (amplitude versus time)

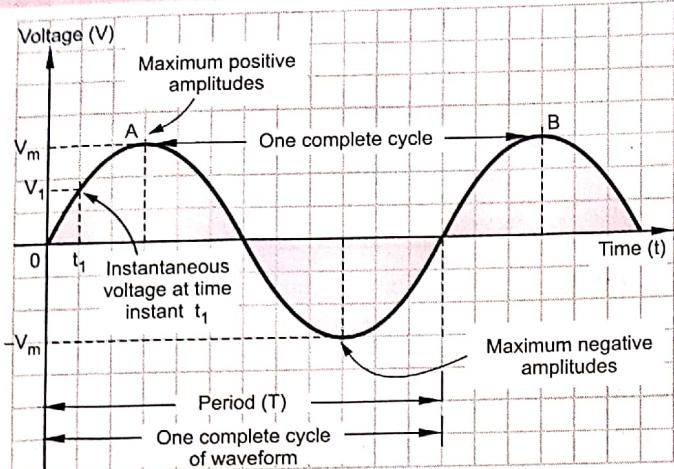

Voltage waveform

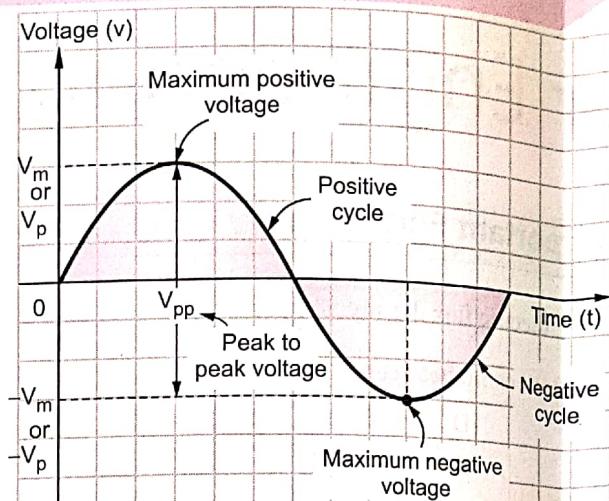

Important Formulae

Summary of some important terms related to alternating quantity.

Sr. No.	Quantity	Notation	Formula	Unit
1.	Period	T	$T = \frac{1}{f}$	Sec
2.	Amplitude	V_m or I_m	V_m or I_m = Peak value	Voltage or ampere
3.	Frequency	f	$f = \frac{1}{T}$	Cycles/sec or Hz
4.	Electric angle	θ	$\theta = 360^\circ$ or 2π radian for one complete revolution.	degree or radian
5.	Angular velocity	ω	$\omega = 2\pi f$	rad/sec

The following table shows different forms of equations of voltage and current

Equations of voltage	Equations of current
(i) $e = E_m \sin(\omega t)$ or $V = V_m \sin(\omega t)$	(i) $i = I_m \sin(\omega t)$
(ii) $e = E_m \sin(2\pi ft)$ or $V = V_m \sin(2\pi ft)$	(ii) $i = I_m \sin(2\pi ft)$
(iii) $e = E_m \sin\left(\frac{2\pi t}{T}\right)$ or $V = V_m \sin\left(\frac{2\pi t}{T}\right)$	(iii) $i = I_m \sin\left(\frac{2\pi t}{T}\right)$


Summary of Important Parameters

Sr. No.	Quantity	Notation	Basic equation	Unit
1.	Peak to peak value	V_{P-P}	$V_{P-P} = 2 \times$ Maximum value	Volts
2.	rms value	V_{rms} or I_{rms}	$0.707 \times$ Maximum value	Volts or ampere
3.	Average value	V_{av} or I_{av}	$0.637 \times$ Maximum value	Volts or ampere
4.	Form factor	K_F	$K_F = \frac{\text{rms value}}{\text{average value}}$	Unitless
5.	Crest factor	K_P	$K_P = \frac{\text{Peak value}}{\text{rms value}}$	Unitless


Chapter 4 (Unit III)

Single Phase AC Circuits


Voltage current and power waveform

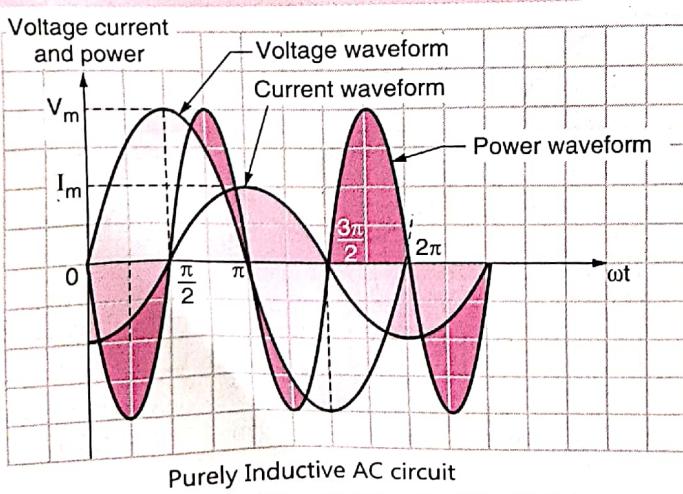


Voltage current and power waveforms

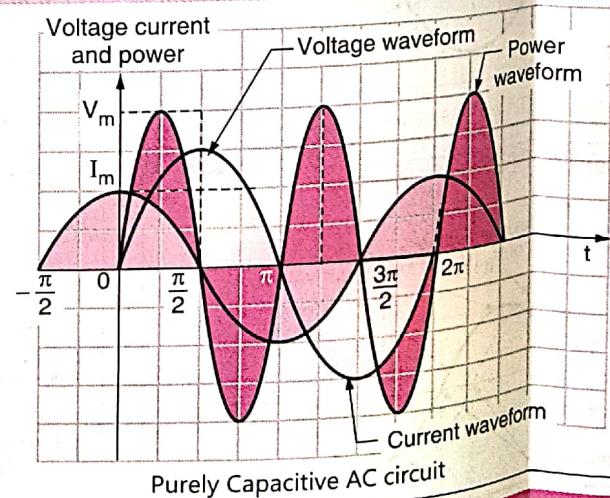

Voltage, current and power waveforms

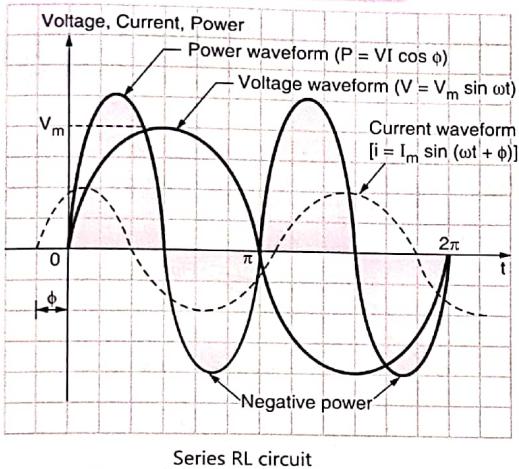

Phasor diagram for RLC circuit

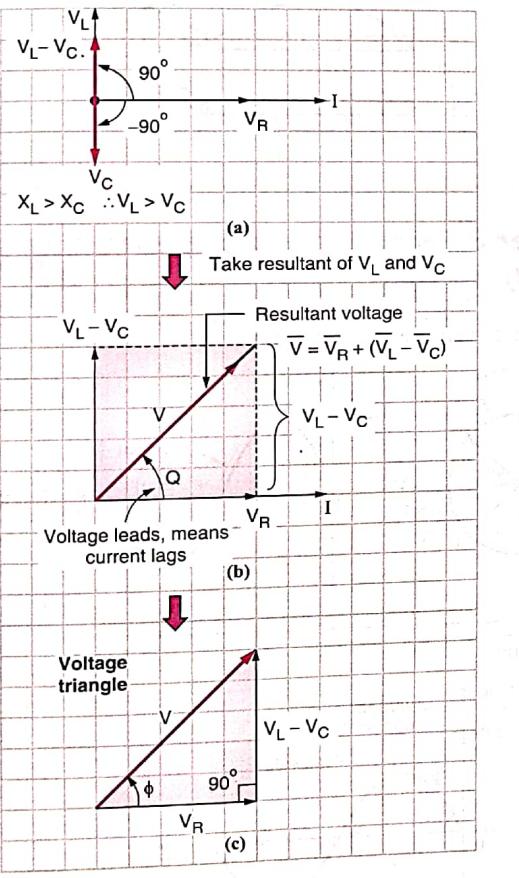

Important Formulae

Expression for Purely Resistive AC Circuit

1. Average power (P_{av})
 $\therefore P_{av} = V_{RMS} I_{RMS}$ watts

Expression for Purely Inductive AC Circuit

2. Voltage applied to purely inductive circuit
 $V = V_m \sin \omega t$

3. Equation of current

$$i = I_m \sin(\omega t - \frac{\pi}{2})$$

Peak value Phase shift
Lagging phase

$$\text{Here, } I_m = \frac{V_m}{X_L};$$

Where $X_L = \text{Reactance of inductor} = \omega L = 2\pi f L$

4. Instantaneous power (P)

$$\therefore P = v \times i$$

Instantaneous voltage Instantaneous current

5. Average Power (P_{av})
 $\therefore P_{av} = 0$

Expression for Purely Capacitive AC Circuit

1. Equation of current

$$i = I_m \sin(\omega t + \frac{\pi}{2})$$

Lagging phase Phase shift

2. Voltage applied to purely capacitive circuit
 $V = V_m \sin \omega t$

3. Basic equation of X_C

$$\therefore X_C = \frac{1}{2\pi f C}$$

Value of capacitance (constant)
Constant Frequency (variable)

4. Instantaneous power

$$\therefore P = v \times i$$

Instantaneous current
Instantaneous voltage

5. Average power (P_{av})

$$\therefore P_{av} = 0$$

Types of power in AC circuits

1. Apparent power (S)

$$S = V_{RMS} \times I_{RMS}$$

2. Real or True or Active power (P)

$$P = V I \cos \phi$$

Real power rms voltage
rms current phase between voltage and current

3. Imaginary or Reactive Power (Q)

$$Q = V I \sin \phi$$

Reactive power rms voltage
rms current phase between voltage and current

4. Range of Power Factor

$$\text{P.F.} = \cos \phi$$

Expressions for RL circuits

1. Equation of supply voltage
 $V = V_m \sin \omega t$

2. Instantaneous current

$$i = I_m \sin(\omega t - \phi)$$

Instantaneous current Peak amplitude
Phase shift Lagging

3. Instantaneous power

$$\therefore P = \frac{V_m I_m \cos \phi}{2} - \frac{V_m I_m}{2} \cos(2\omega t - \phi)$$

Phase shift
Lagging
Constant term as ϕ is constant Double frequency

4. Average power

$$\therefore P_{av} = VI \cos \phi$$

Expressions for RC circuits

1. Equation of supply voltage
 $V = V_m \sin \omega t$

2. Instantaneous current

$$i = I_m \sin(\omega t + \phi)$$

Instantaneous current Peak amplitude
Phase shift Leading

3. Instantaneous power

$$\therefore P = V_m \sin(\omega t) \cdot I_m \sin(\omega t + \phi)$$

4. Average power


$$\therefore P_{av} = VI \cos \phi$$

Types of power in AC circuits


1. Apparent power (S)

$$S = V_{\text{RMS}} \times I_{\text{RMS}}$$

2. Real or True or Active power (P)

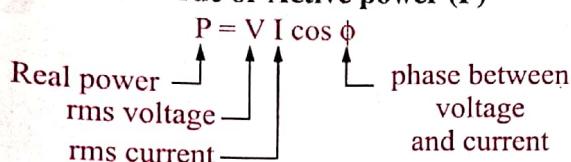

3. Imaginary or Reactive Power (Q)

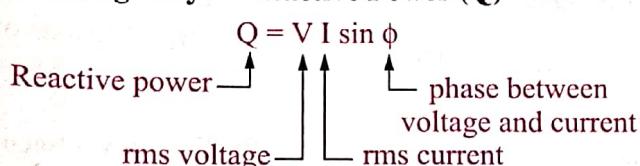

4. Range of Power Factor


$$\text{P.F.} = \cos \phi$$

Expressions for RL circuits

1. Equation of supply voltage

$$V = V_m \sin \omega t$$

2. Instantaneous current

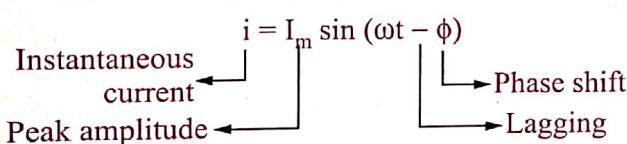

3. Instantaneous power

$$\therefore P = \frac{V_m I_m \cos \phi}{2} - \frac{V_m I_m}{2} \cos(2\omega t - \phi)$$

Constant term as ϕ is constant Double frequency

Phase shift Lagging

4. Average power


$$\therefore P_{av} = VI \cos \phi$$

Expressions for RC circuits

1. Equation of supply voltage

$$V = V_m \sin \omega t$$

2. Instantaneous current

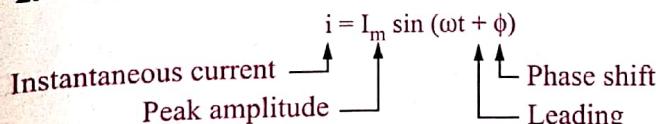

3. Instantaneous power

$$\therefore P = V_m \sin(\omega t) \cdot I_m \sin(\omega t + \phi)$$

4. Average power

$$\therefore P_{av} = VI \cos \phi$$

Expressions for RLC circuits

1. Nature of Power Factor

Following table shows the nature of power factor.

Serial No.	Condition	Type of RLC circuit	Nature of power factor
1.	$X_L > X_C$	Inductive	Leading and less than 1
2.	$X_L < X_C$	Capacitive	Leading and less than 1
3.	$X_L = X_C$	Resistive	Equal to 1

2. Q factor in RLC series circuit

$$Q = \frac{X}{R}$$

Resistance

Rectance

Here $X = X_L - X_C$

Inductive reactance

Capacitive reactance

Expressions on series resonance

1. Resonant Frequency

$$\therefore f_r = \frac{1}{2\pi\sqrt{LC}} \text{ (Hz) Unit}$$

2. Impedance of Series Resonant Circuit

$$\therefore Z = R + j(X_L - X_C)$$

3. Bandwidth (B.W.) of Series Resonance

$$\therefore B.W. = f_2 - f_1$$

4. Selectivity

$$\therefore S = \frac{f_r}{B.W.}$$


5. Quality Factor (Q-factor) of Series Resonant Circuit

$$Q = \frac{1}{R} \sqrt{\frac{L}{C}}$$


6. Relation between Q and bandwidth

$$\therefore Q = \frac{f_r}{B.W.}$$


Winding is rotating

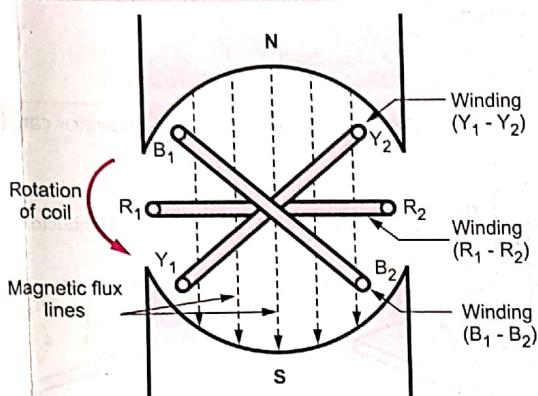


Balances star connected load

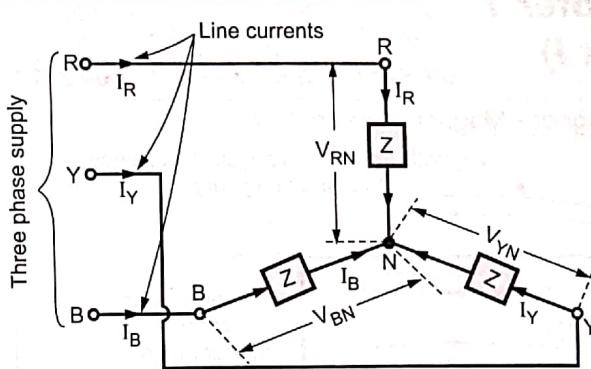


Types of load connections

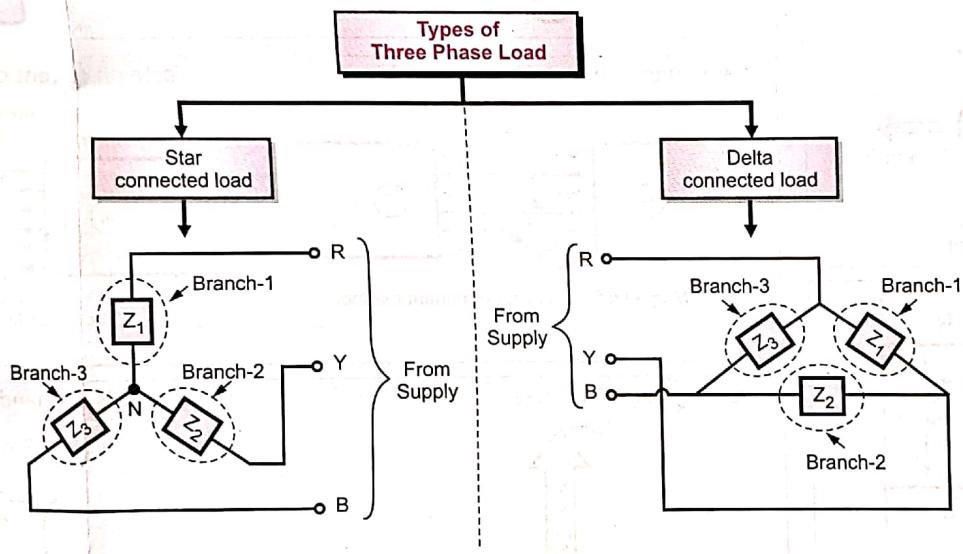


Field is rotating

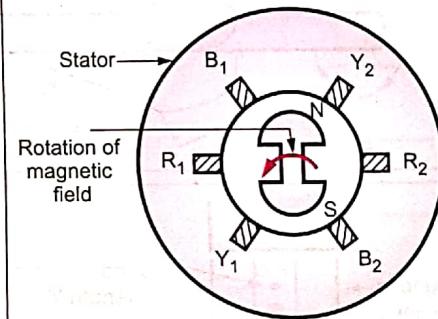

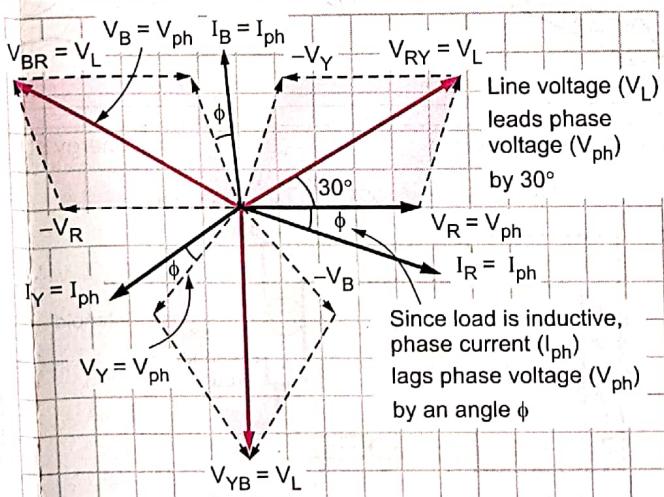Complete phasor diagram per star connection



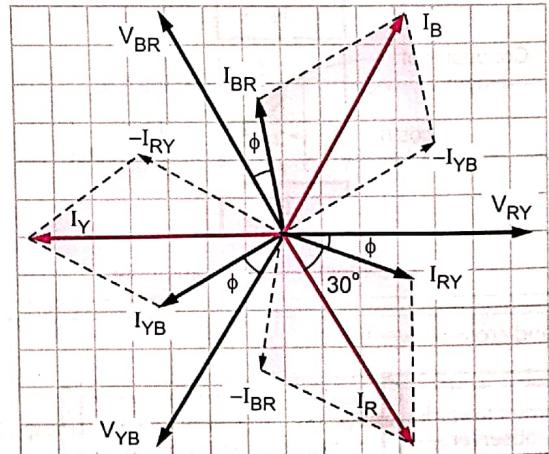Complete Phasor Diagram for delta connection



Important Formulae

Relationship for balanced star connected load

- The line current is same as phase current. That means,
 $I_L = I_{ph}$
- The line voltage is $\sqrt{3}$ times the phase voltage. That means,
 $V_L = \sqrt{3} V_{ph}$
- The line voltage leads the phase voltage by 30° .

Summary of equations of power

The following table shows summary of mathematical equations of different powers.


Sr. No.	Type of power	Unit	Equation in terms of phase voltage and current	Equation in terms of line voltage and current
1.	Apparent power (s)	VA	$s = 3 V_{ph} \cdot I_{ph}$	$s = \sqrt{3} V_L \cdot I_L$
2.	Active power (P)	W	$P = 3 V_{ph} \cdot I_{ph} \cos \phi$	$P = \sqrt{3} V_L \cdot I_L \cos \phi$
3.	Reactive power (Q)	VAR	$Q = 3 V_{ph} \cdot I_{ph} \sin \phi$	$Q = \sqrt{3} V_L \cdot I_L \sin \phi$

$$\text{Power Factor (P.F.) } \therefore \text{P.F.} = \cos \phi$$


Chapter 6 (Unit IV)

Single Phase Transformer


Basic transformer

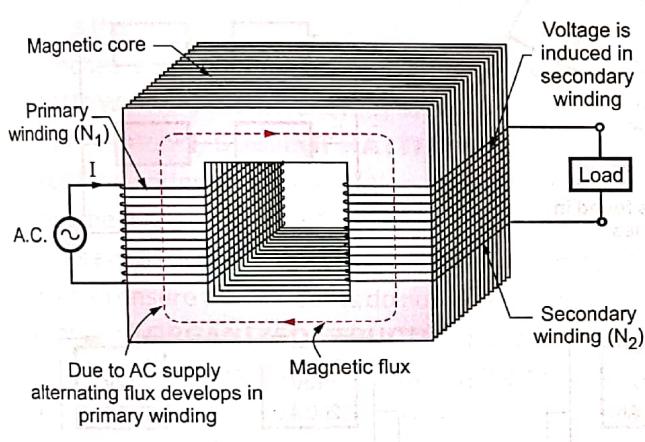


Types of transformer

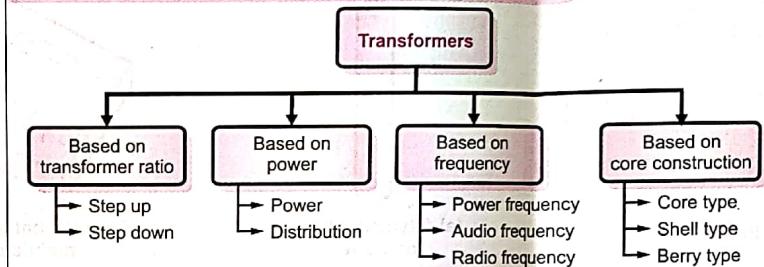

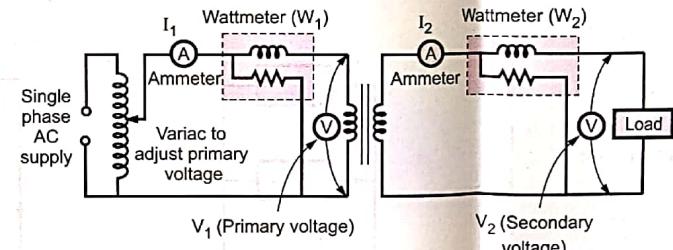
Experimental setup for direct loading method




Transformer losses

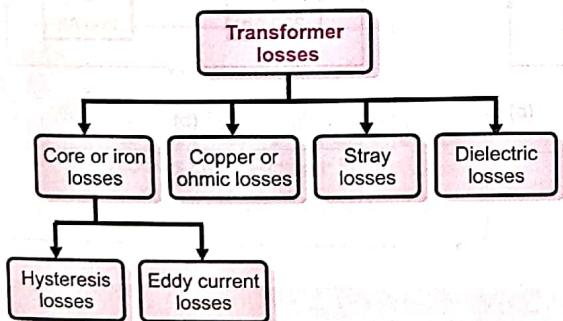


Basic auto transformer

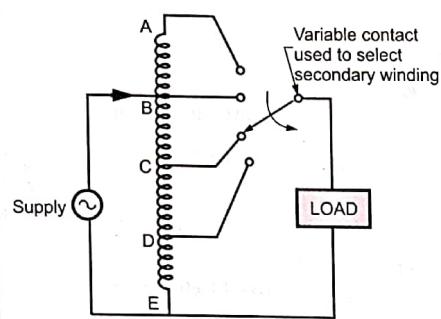

Symbol

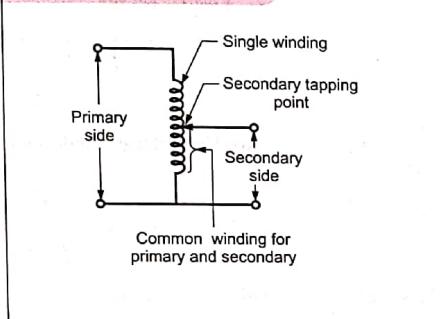

Symbol of transformer

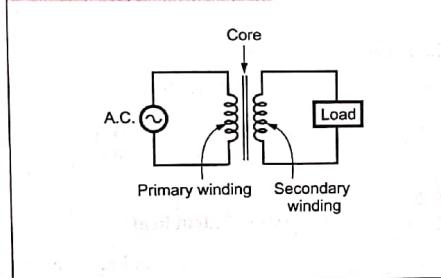

Important Formulas

EMF and Transformer Ratios

- Induced emf (e) is given by,
Number of turns of coil \downarrow Rate of change of flux \downarrow
$$e = -N \frac{d\phi}{dt}$$

- Maximum value of e
 $\therefore e_{\max} = N \Phi_m 2\pi f$ volt
 $\therefore e_{\max} = \Phi_m 2\pi f$ volts

Above equation gives maximum value of induced emf per turn.

- Above equation gives rms value of induced emf per turn.
 $\therefore E_1 = 4.44 \Phi_m \cdot f N_1$
and $E_2 = 4.44 \Phi_m f N_2$

Above equations give the value of statically induced emf in primary and secondary windings respectively.

- e.m.f. / turn for primary $= \frac{E_1}{N_1} = 4.44 f \Phi_m$
and e.m.f. / turn for secondary $= \frac{E_2}{N_2} = 4.44 f \Phi_m$
 $\therefore \text{emf ratio} = \frac{E_1}{E_2} = \frac{N_1}{N_2}$

5. Voltage ratio without load

$$\therefore V_2 = E_2$$

Load voltage \uparrow Secondary induced voltage \uparrow
Secondary terminal voltage at no load Secondary terminal voltage at given load

6. Primary terminal voltage

$$\therefore V_1 \approx E_1$$

Primary terminal voltage \uparrow Primary induced voltage \uparrow

1. Calculation of efficiency (η)

$$\eta = \frac{\text{Output power } (W_2)}{\text{Input power } (W_1)} \times 100 \%$$

$$8. \text{ Voltage Ratio : } \frac{V_1}{V_2} = \frac{N_1}{N_2}$$

$$9. \text{ Transformation ratio : } K = \frac{V_2}{V_1} = \frac{N_2}{N_1}$$

$$10. \text{ Current ratio : } \frac{I_1}{I_2} = \frac{V_2}{V_1} = \frac{N_2}{N_1} = K$$

11. Equations of full load currents

$$I_1 (\text{full load}) = \frac{k \text{VA rating} \times 1000}{V_1}$$

$$\text{and } I_2 (\text{full load}) = \frac{k \text{VA rating} \times 1000}{V_2}$$

12. The transformer ratings are specified in the following format.

Primary voltage/secondary voltage, kVA rating, supply frequency.

Efficiency

- Power loss in primary winding $= I_1^2 R_1$

and power loss in secondary winding $= I_2^2 R_2$

Copper loss $\therefore P_{cu} = I_1^2 R_1 + I_2^2 R_2$

Thus total losses $=$ Iron loss (P_i) + Copper loss (P_{cu})

- The generalized equation of efficiency is,

$$\eta = \frac{n (\text{VA}) \cos \phi}{n (\text{VA}) \cos \phi + P_i + n^2 P_{cu}} \times 100 \%$$

- The condition for maximum efficiency is,

$$P_i = P_{cu}$$

- Mathematically, voltage regulation is expressed as,

Secondary terminal voltage at no load \downarrow Secondary terminal voltage at given load \downarrow

$$\% \text{ Voltage regulation} = \frac{E_2 - V_2}{E_2} \times 100$$

Direct loading method

1. Calculation of efficiency (η)

$$\eta = \frac{\text{Output power } (W_2)}{\text{Input power } (W_1)} \times 100 \%$$

Input current \downarrow Input voltage \downarrow Output voltage \downarrow
Input power \downarrow P.F. \downarrow Output power \downarrow P.F.

Here $W_1 = V_1 I_1 \cos \phi_1$, $W_2 = V_2 I_2 \cos \phi_2$














2. Calculation of regulation (R)

Percentage regulation =


$$\frac{\text{No load output voltage } (V_{2NL}) - \text{Full load output voltage } (V_{2FL})}{\text{No load output voltage } (V_{2NL})} \times 100 \%$$

$$\therefore \% R = \frac{V_{2NL} - V_{2FL}}{V_{2NL}} \times 100 \%$$


Chapter 7 (Unit V) DC Circuits

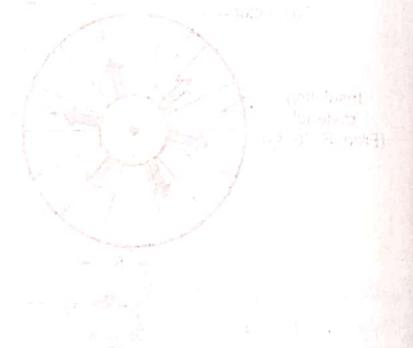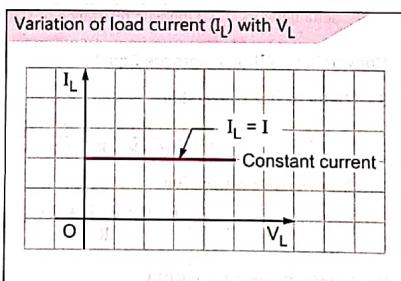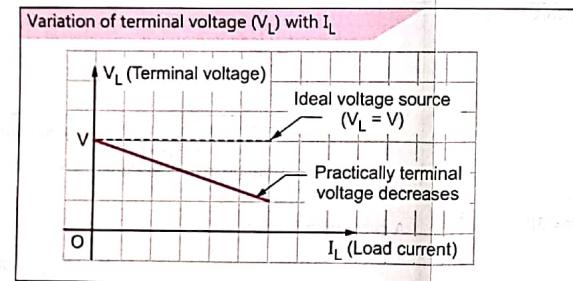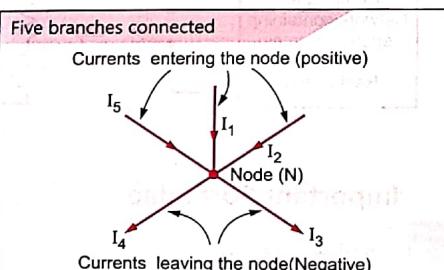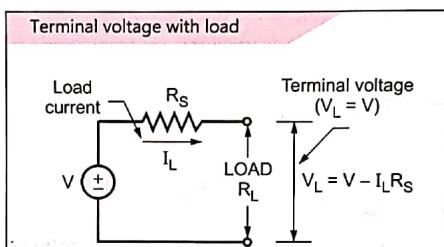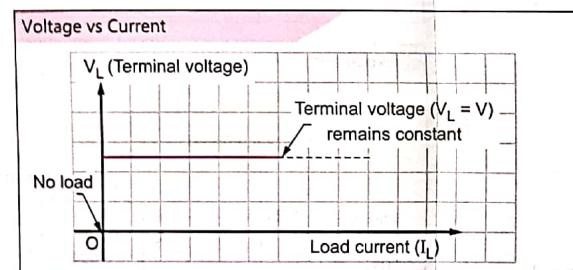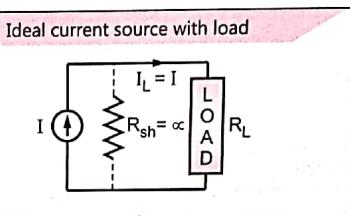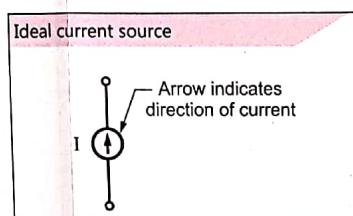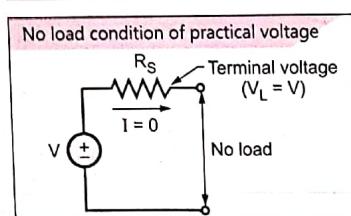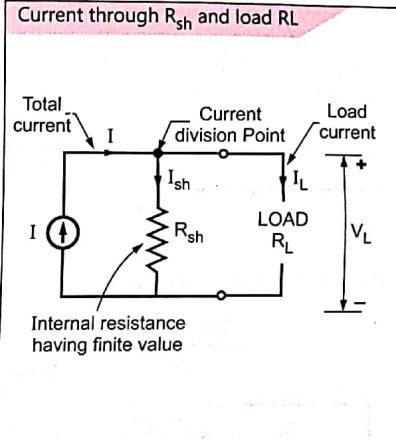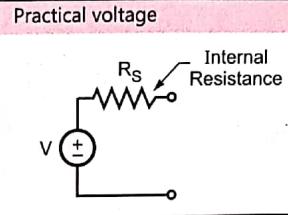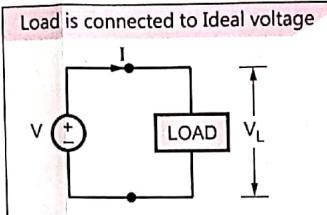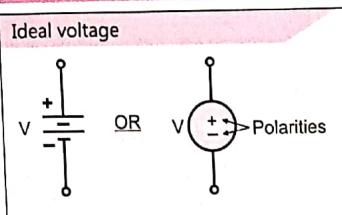


Delta to star conversion

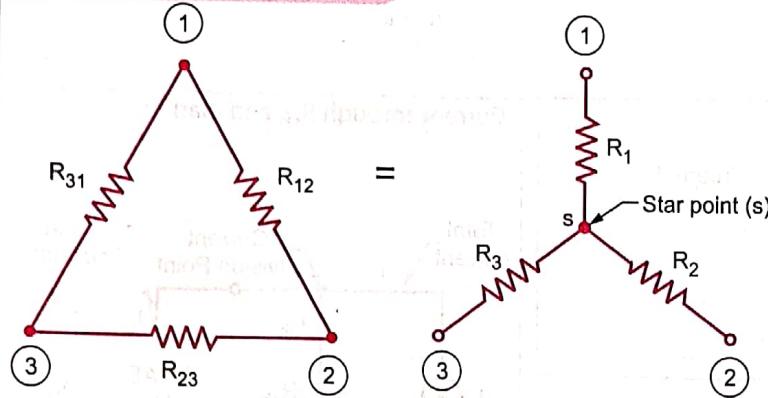

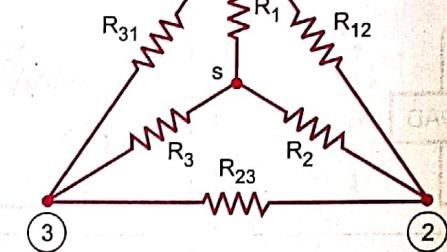Delta network to be converted into star
Converted star network



Thevenin's equivalent resistance

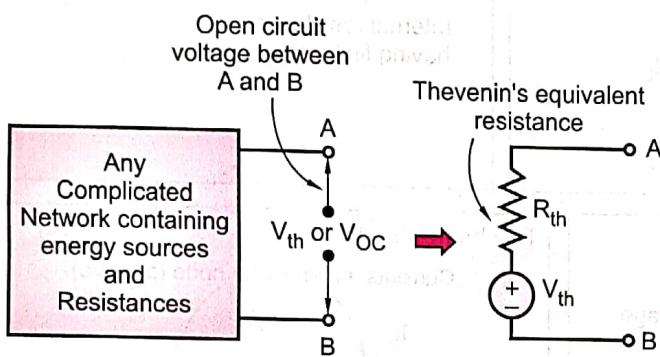

Important Formulae

1. Resistors in Series

If 'n' resistors are connected in series then equivalent resistance is,

$$R_T = R_1 + R_2 + \dots + R_n$$

2. Voltage Division formula

Voltage across any resistance = $\frac{\text{Supply voltage} \times \text{that resistance}}{\text{Addition of all resistances}}$

3. Resistors in Parallel

In general, if 'n' resistors are connected in parallel then total resistance is,

$$\frac{1}{R_T} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} + \dots + \frac{1}{R_n}$$

4. Case of Two Resistances in Parallel

Equivalent resistance (R_T) = $\frac{\text{Multiplication of resistances}}{\text{Addition of two resistances}}$

5. Current Division in Parallel Circuit

Current in any branch = $\frac{\text{Total current} \times \text{Opposite branch resistance}}{\text{Addition of resistances}}$

1. To convert delta network into star network

Any resistance in star network = $\frac{\text{Product of adjacent resistors in delta network}}{\text{Addition of all resistors in delta network}}$

2. To convert star network into delta network

Any resistance in delta network = $\frac{\text{Total resistance } (R_T) \text{ of star network}}{\text{Opposite resistance of star network}}$

Conversion if All Resistors are Equal

3. Delta to star conversion

Any resistance in star = $\frac{R \cdot R}{R + R + R} = \frac{R^2}{3R} = \frac{R}{3}$

4. Star to delta conversion

Any resistance in delta = $\frac{R \cdot R + R \cdot R + R \cdot R}{R} = \frac{3R^2}{R} = 3R$

Kirchhoff's Current Law (KCL)

Summation of incoming currents = Summation outgoing currents

$$\underbrace{I_1 + I_2 + I_3}_{\text{Current entering the node}} = \underbrace{I_3 + I_4}_{\text{Current leaving the node}}$$


Kirchhoff's Voltage Law (KVL)

Around a closed path \sum voltage across all elements = 0


Current in any branch = $\frac{\text{Supply current} \times \text{Opposite branch resistance}}{\text{Addition of resistances}}$

Voltage across any resistor = $\frac{\text{Supply voltage} \times \text{that resistor}}{\text{Addition of resistors}}$

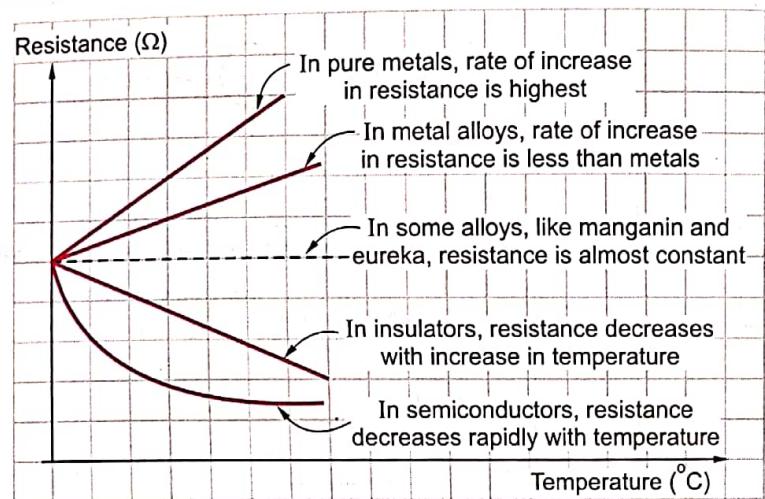
Concept of decrease in resistance in semiconductor



Explanation of RTC

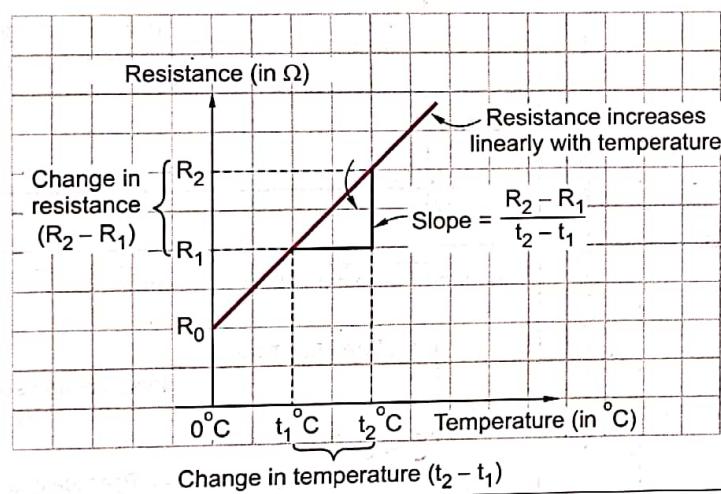

A cable with insulator

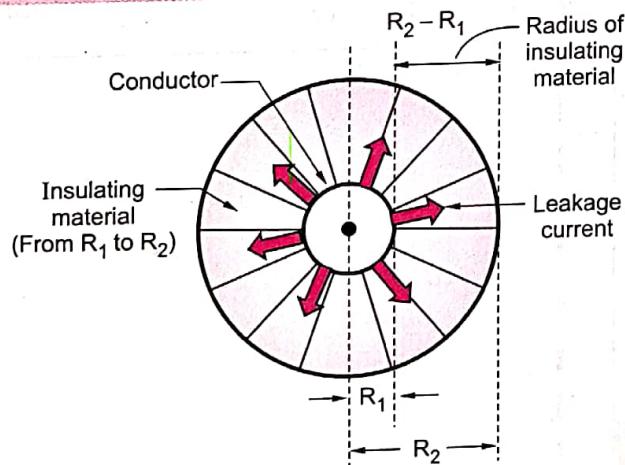

Important Formulae

(i) Equation of resistance temperature coefficient at $t_1^{\circ}\text{C}$ (α_1)

$$\alpha_1 = \frac{(R_2 - R_1) / (t_2 - t_1)}{R_1}$$

Where, R_1 = Resistance at $t_1^{\circ}\text{C}$, R_2 = Resistance at $t_2^{\circ}\text{C}$
 α_1 = RTC at $t_1^{\circ}\text{C}$

(ii) Equation of RTC at 0°C (α_0)

$$\alpha_0 = \frac{(R_1 - R_0) / (t_1 - 0)}{R_0}$$

Where, R_1 = Resistance at $t_1^{\circ}\text{C}$, R_0 = Resistance at $t_0^{\circ}\text{C}$
 α_0 = RTC at $t_0^{\circ}\text{C}$

(iv) Equation of Resistance in Terms of RTC

$$\text{Resistance at } t_1^{\circ}\text{C} \quad \downarrow \quad \text{RTC at } t_1^{\circ}\text{C} \quad \downarrow$$

$$\therefore R_2 = R_1 [1 + \alpha_1 (t_2 - t_1)]$$

$$\text{Resistance at } t_2^{\circ}\text{C} \quad \uparrow \quad \text{Temperature difference}$$

(v) Effect of Temperature on RTC (α_t)

$$\therefore \alpha_t = \frac{\alpha_0}{1 + \alpha_0 t}$$

Where, α_t = RTC at $t^{\circ}\text{C}$, α_0 = RTC at 0°C

(vi) Temperature Coefficient of Resistivity

$$\text{Resistivity at } t_1^{\circ}\text{C} \quad \downarrow \quad \text{Resistivity at } t_0^{\circ}\text{C} \quad \downarrow$$

$$\alpha_0 = \frac{(\rho_1 - \rho_0) / (t_1 - 0)}{\rho_0}$$

Change in temperature

(vii) Composite temperature coefficient (α)

$$\therefore \alpha = \frac{R_1 \alpha_1 + R_2 \alpha_2}{R_1 + R_2}$$

Where, R_1 = Resistance of material 1
 R_2 = Resistance of material 2
 α_1 = Temperature coefficient material 1
 α_2 = Temperature coefficient material 2

(i) Relation between resistance (R) and resistivity (ρ) is,

Resistivity \downarrow Length

$$R = \frac{\rho l}{a}$$

Resistance \uparrow Cross sectional area

(ii) Resistivity

$$\text{Resistivity} \downarrow \\ \therefore R_i = \frac{\rho}{2\pi l} \log_e \frac{(R_2)}{(R_1)} \quad \begin{array}{l} \text{Radius (Conductor} \\ + \text{insulator}) \\ \downarrow \\ (R_2) \\ \uparrow \\ (R_1) \end{array}$$

Length \uparrow

Radius of conductor \downarrow

(i) Force

$$F = m \times a \quad \begin{array}{l} \text{Mass} \\ \downarrow \\ \text{Force} \\ \uparrow \\ \text{Acceleration} \end{array}$$

(ii) Weight

$$W = m \times g \quad \begin{array}{l} \text{Mass} \\ \downarrow \\ \text{Weight} \\ \uparrow \\ \text{Gravitational} \\ \text{acceleration} = 9.81 \text{ m/s}^2 \end{array}$$

(iii) Torque

$$T = F \times r \quad \begin{array}{l} \text{Force} \\ \downarrow \\ \text{Torque} \\ \uparrow \\ \text{Radial distance} \end{array}$$

(iv) Work

$$W = F \times d \quad \begin{array}{l} \text{Force} \\ \downarrow \\ \text{Workdone} \\ \uparrow \\ \text{Displacement} \end{array}$$

(v) Kinetic energy

$$\text{K.E.} = \frac{1}{2} m V^2 \quad \begin{array}{l} \text{Mass} \\ \downarrow \\ \frac{1}{2} \\ \uparrow \\ \text{Velocity} \end{array}$$

(vi) Potential energy

$$\text{P. E.} = m g h \quad \begin{array}{l} \text{Mass} \\ \downarrow \\ \text{Height} \\ \uparrow \\ \text{Gravitational force} \end{array}$$

(vii) Power

$$\text{Power} \quad \begin{array}{l} \text{Angular velocity} \\ \downarrow \\ \therefore P = \omega T \\ \uparrow \\ \text{Torque} \end{array}$$

(viii) Electrical work

$$\text{Electric work} \quad \begin{array}{l} \text{Charge} \\ \downarrow \\ W = V \cdot Q \quad \text{J} \\ \uparrow \\ \text{Potential difference} \\ \uparrow \\ \text{Unit of work done} \\ (\text{Joules}) \end{array}$$

(ix) Electric power

$$\text{Electric power} \quad \begin{array}{l} \text{Voltage} \\ \downarrow \\ \therefore P = V I \quad \text{Watts} \\ \uparrow \\ \text{Current} \end{array}$$

(x) Electric energy

$$\text{Energy} \quad \begin{array}{l} \text{Power} \\ \downarrow \\ \therefore E = P \times t \\ \uparrow \\ \text{Time} \end{array}$$

(xi) Heat energy (Joule's law)

$$\text{Heat energy (H)} = V I t \quad \begin{array}{l} \text{Current} \\ \downarrow \\ \text{Voltage} \\ \uparrow \\ \text{Time} \end{array}$$

(xii) Specific heat

$$C = \frac{Q}{m(t_2 - t_1)} \quad \begin{array}{l} \text{Heat supplied} \\ \downarrow \\ \text{Mass of body} \\ \uparrow \\ \text{Change in temperature} \end{array}$$

(xiii) Sensible heat

$$\text{Sensible heat} = m C (t_2 - t_1) \quad \begin{array}{l} \text{Mass} \\ \downarrow \\ \text{Specific heat} \\ \uparrow \\ \text{Change in temperature} \end{array}$$

(xiv) Latent heat

$$\text{Latent heat} = m \cdot L \quad \begin{array}{l} \text{Mass of substance} \\ \uparrow \\ \text{Specific latent heat} \\ \text{or enthalpy} \end{array}$$

(xv) Efficiency of System


$$\eta = \frac{\text{Energy Output}}{\text{Energy Input}} \times 100\%$$

$$\text{OR } \eta = \frac{\text{Power Output}}{\text{Power Input}} \times 100\%$$

Chapter 9 (Unit VI)

Batteries


lead Acid Battery

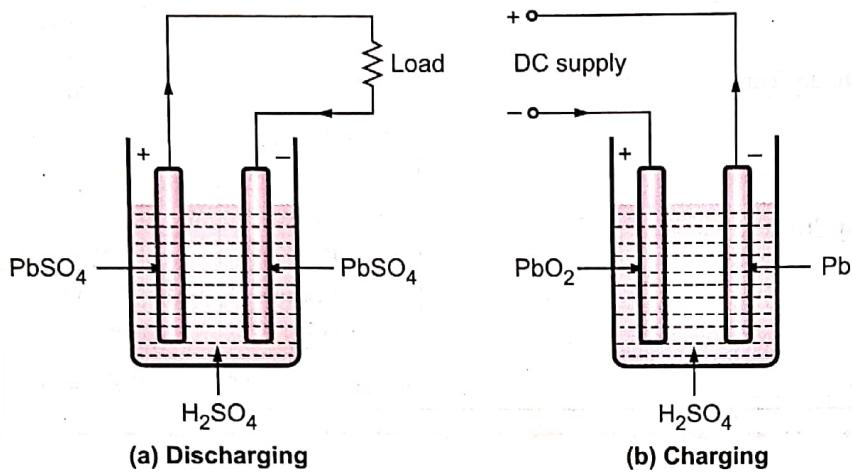

Types of lithium ion batteries





(a) A typical lithium ion battery

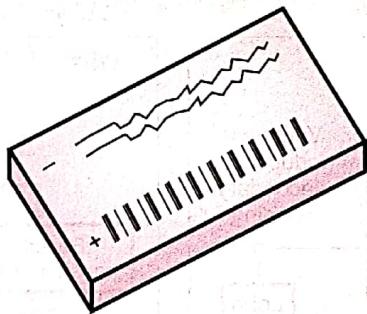


(b) Li ion batteries found in mobile phones

Series connection of batteries

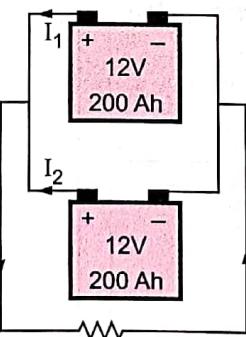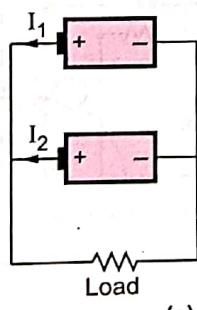



(b)

Parallel connection of batteries

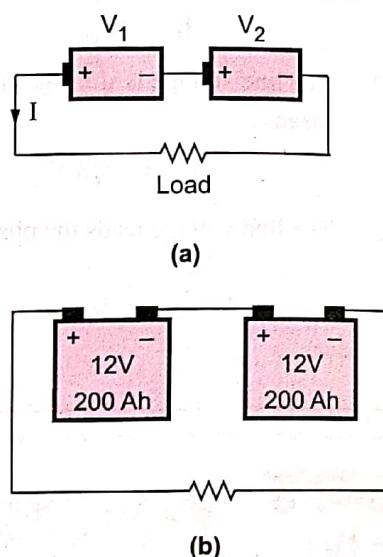

(b)

Series parallel connection of batteries

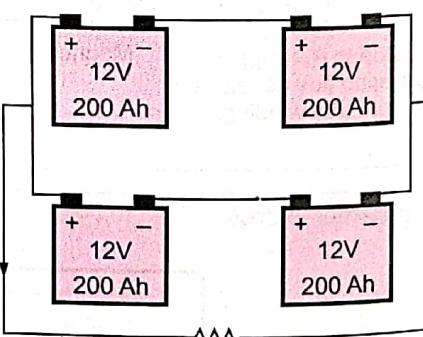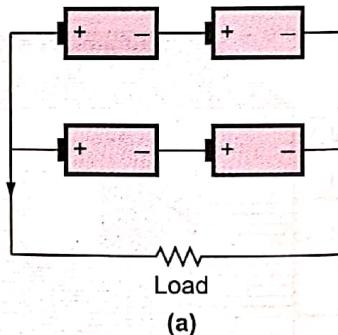

(b)